
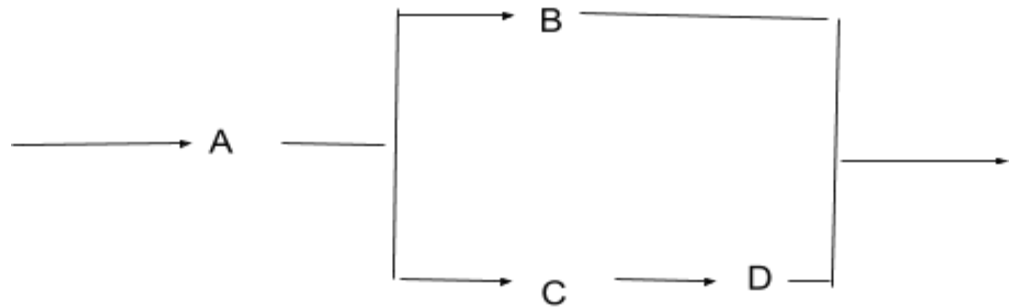


From the given network, write a Boolean expression that represents it:


1.

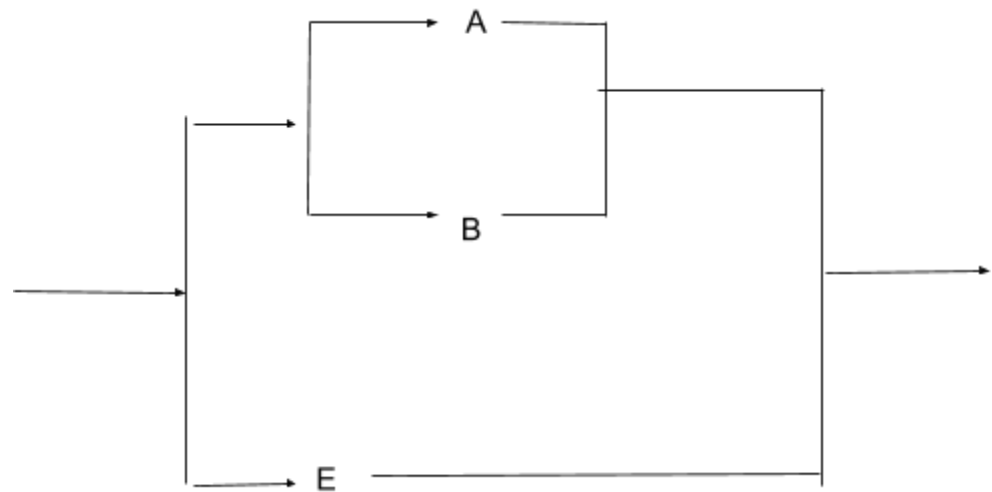

2.



3.

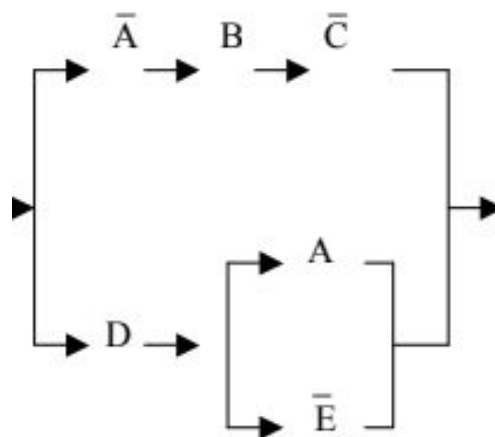

Draw a network to represent each Boolean expression:

4. $ABCD$

5. $AB+AC$

6. $(A+B)(A+C)$

7. $A+B(C+D)$

8. $AB(C+D)E$

9. $(A+B)(D+EF)$

10. $AB(DAE+\bar{A}C)$